



United International University
QUEST FOR EXCELLENCE



CSE 1326: Digital Logic Design Lab

Decoders

United International University

What to do (skip grayed colored ones)

1. Implementation: Implement 3-to-8 line decoder using


- a) Basic gates, AND gate with more inputs - Non-hierarchical
- b) Decoder and two-input AND gates - Hierarchical (LS)
- c) 2-to-4 line decoders with enable (Both TB and LS)

2. Application: Implement combinational circuits (functions) using decoder and basic gates

$$F = M_1 \cdot M_3 \cdot M_6 \cdot M_7$$

What To Do (1c)

 1c) Implement a 3-to-8 line decoder using 2-to-4 line decoders with enable (see below) – Both TB and LS.



IC: 74139 dual 2-to-4 Decoder



Function Table of 74LS139

| INPUTS | | | OUTPUTS | | | |
|--------|--------|---|---------|----|----|----|
| Enable | Select | | | | | |
| G | B | A | Y0 | Y1 | Y2 | Y3 |
| 1 | X | X | 1 | 1 | 1 | 1 |
| 0 | 0 | 0 | 0 | 1 | 1 | 1 |
| 0 | 0 | 1 | 1 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 | 1 | 1 | 0 |

1 = High, 0 = Low, X = don't care



| PIN NO. | SYMBOL | NAME AND FUNCTION |
|---------------|------------------------------|----------------------------|
| 1, 15 | $1\bar{E}, 2\bar{E}$ | enable inputs (active LOW) |
| 2, 3 | $1A_0, 1A_1$ | address inputs |
| 4, 5, 6, 7 | $1\bar{Y}_0$ to $1\bar{Y}_3$ | outputs (active LOW) |
| 8 | GND | ground (0 V) |
| 12, 11, 10, 9 | $2\bar{Y}_0$ to $2\bar{Y}_3$ | outputs (active LOW) |
| 14, 13 | $2A_0, 2A_1$ | address inputs |
| 16 | V_{CC} | positive supply voltage |

Functional/Pin Diagram

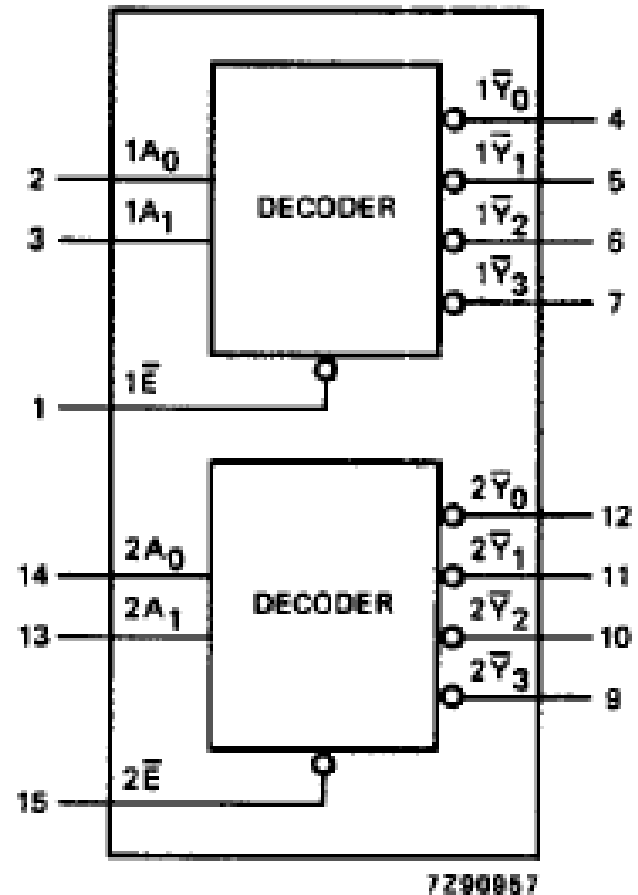 

Implement a 3-to-8 line Decoder

  - Following that pattern complete this connection using 74139, note the pin numbers



What To Do (2)

2. Application: Implement combinational circuits (functions) using decoder and basic gates.

$$F = M_1 \cdot M_3 \cdot M_6 \cdot M_7$$

- a) For trainer board, use the circuit in 1c.
- b) For LS, use SOM, $F = m_0 + m_2 + m_4 + m_5$

- Active-low decoders generate maxterms.
- If you have a product of maxterms equation for a function, you can easily use a active-low decoder and AND gates to implement that function.
- But, in logisim, there is no Active-low decoder. What can we do?

Writing Report (skip grayed colored ones)

1. Pin diagram of 74139 (with two 2-to-4 decoders inside).
 2. Logic diagram of 3-to-8 line decoder implementation
 - a) Basic gates, non-hierarchical (AND gate more inputs)
 - b) Basic gates, hierarchical (Decoder and AND gate – two inputs)
 - c) 2-to-4 line decoders with enable
 3. Logic diagram of realizing combinational circuits using 3-to-8 line decoder
- Answer the question: How to use the 3-to-8 line decoder (the one you have designed with two 2-to-4 line decoders) for implementing the following function?

$$F = M_1 \cdot M_3 \cdot M_6 \cdot M_7$$

$$F = m_0 + m_4 + m_5 + m_7$$