



United International University
QUEST FOR EXCELLENCE



CSE 1326: Digital Logic Design Lab

Multiplexers

United International University

Objective


- **Study** 4-input and 8-input multiplexers (MUX)
- **Application:** Design and implement the Boolean Function
 - $F(A,B,C) = \sum_m (0, 1, 4, 7) = \sum_m (1, 3, 4, 6)$

Using

1. 8 input MUX and necessary basic gates
2. 4 input MUX and necessary basic gates



74151: 8-input multiplexer

PIN NO.	SYMBOL	NAME AND FUNCTION
4, 3, 2, 1, 15, 14, 13, 12	I_0 to I_7	multiplexer inputs
5	Y	multiplexer output
6	\bar{Y}	complementary multiplexer output
7	\bar{E}	enable input (active LOW)
8	GND	ground (0 V)
11, 10, 9	S_0, S_1, S_2	select inputs
16	V_{CC}	positive supply voltage

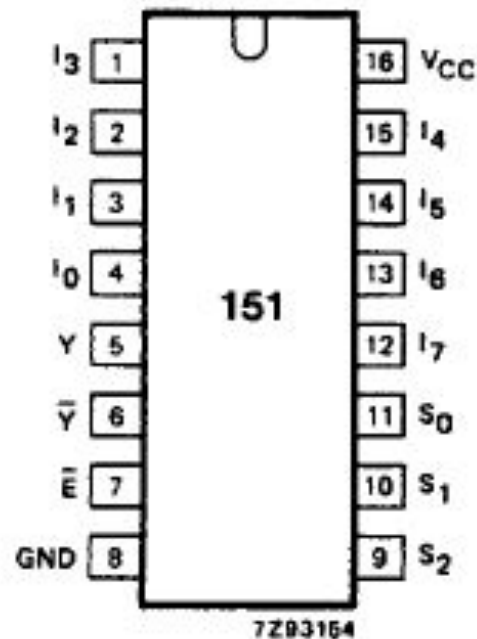

74153: Dual 4-input multiplexer


PIN NO.	SYMBOL	NAME AND FUNCTION
1, 15	$1\bar{E}, 2\bar{E}$	output enable inputs (active LOW)
14, 2	S_0, S_1	common data select inputs
6, 5, 4, 3	$1I_0$ to $1I_3$	data inputs from source 1
7	$1Y$	multiplexer output from source 1
8	GND	ground (0 V)
9	$2Y$	multiplexer output from source 2
10, 11, 12, 13	$2I_0$ to $2I_3$	data inputs from source 2
16	V_{CC}	positive supply voltage

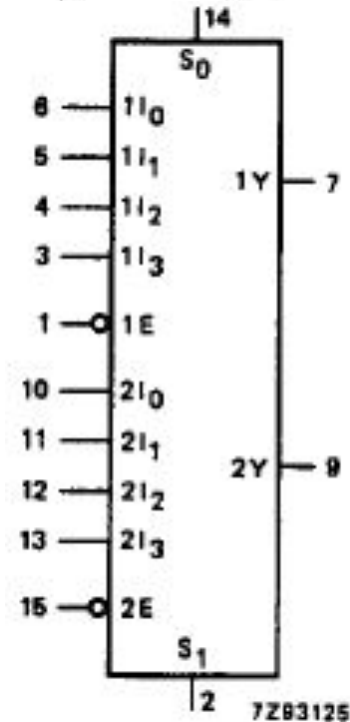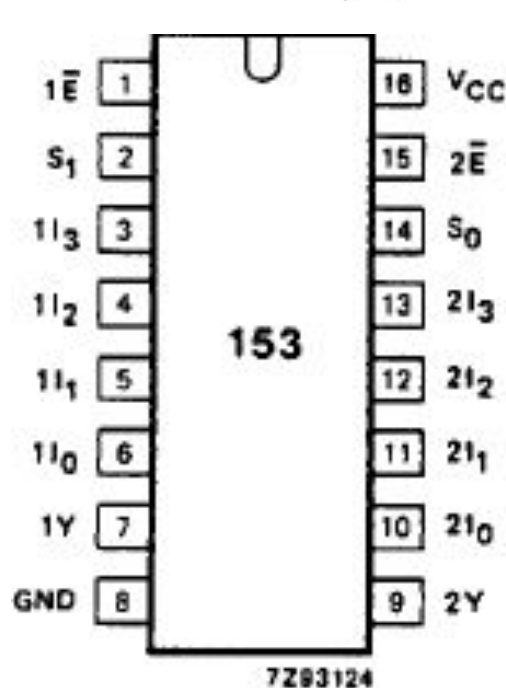

What to do (1)

- Implement $F(A,B,C) = \sum_m (0, 1, 4, 7)$ using 8-input multiplexer


A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

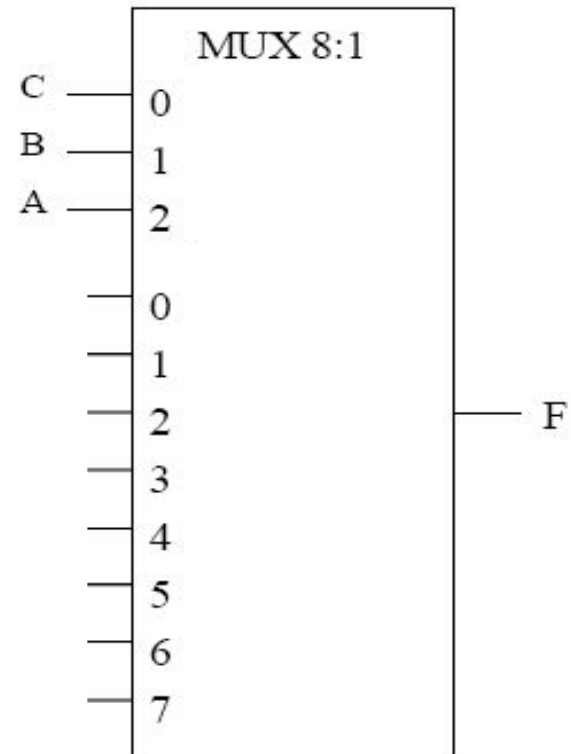

What to do (2)

- Implement $F(A,B,C) = \sum_m (0, 1, 4, 7)$ using 4-input multiplexer

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

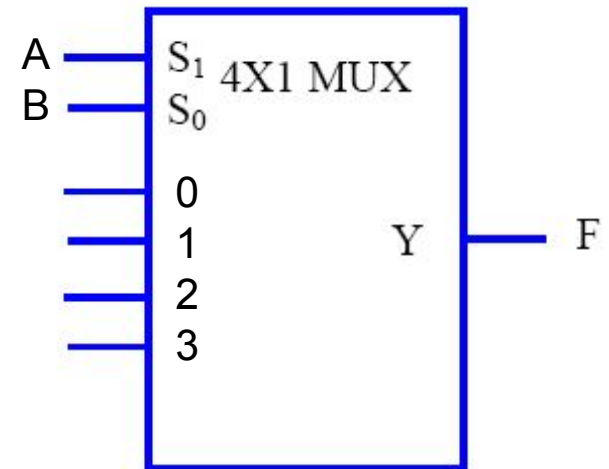

Writing Report

- Provide pin diagram of 74151 and 74153.
- Circuit diagram of implementation of $F(A,B,C) = \sum_m (1, 3, 4, 6)$ using 4 input MUX and necessary basic gates
- Truth table, input functions, and circuit diagram of implementation of the function $F(A,B,C) = \sum_m (1, 3, 4, 6)$ using 2-to-1 MUX and necessary basic gates.